 


①

CLOCKED SR FLIP FLOP



TRUTH TABLE FOR CLOCKED SR FLIP FLOP

	CLK	S	R	S*	R*	Q	\bar{Q}
①	0	X	X	1	1	NO CHANGE	MEMORY (LATCHED)
②	1	0	0	1	1	NO CHANGE	MEMORY (LATCHED)
③	1	0	1	1	0	0	1
④	1	1	0	0	1	1	0
⑤	1	1	1	0	0	INVALID	

METASTABILITY

2

TABLE 1 NAND

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

S-R LATCH (NAND GATES)

\bar{S}	\bar{R}	Q	\bar{Q}
0	0	INVALID	
0	1	1	0
1	0	0	1
1	1	NO CHANGE MEMORY (LATCHED)	

① IF CLOCK IS 0, OUTPUT FROM NAND GATE IS ALWAYS 1 (IRRESPECTIVE OF THE 2ND INPUT)



SO OUTPUTS S^* AND R^* WILL BOTH BE 1.

clk	A	B	Z
0	0	0	1
0	0	1	1

(3)

LINE (2)



CLOCK	S	S*
1	0	1

  

CLOCK	R	R*
1	0	1

LINE (3)

CLOCK	S	R
1	0	1

  

CLOCK	R
1	1

④

THINK THROUGH LAST TWO LINES, LINES 4 AND 5.